

ELEC 374 Digital Systems Engineering Laboratory Project

Winter 2024

Designing a Simple RISC Computer: Phase 3

1. Objectives

The objective of this project is to design, simulate, implement, and verify a simple RISC Computer (Mini SRC). So far, you have designed and functionally simulated the Datapath portion of the Mini SRC (except for *nop* and *halt* instructions that you will test in this phase). Phase 3 of this project consists of adding and testing the Control Unit in Mini SRC. You are to design the Control Unit in Verilog or VHDL. Testing will be done by Functional Simulation.

2. Preliminaries

2.1 Control Unit

A block diagram of the Control Unit for Mini SRC is shown in Figure 1. The Control Unit is at the heart of the processor. It accepts as input those signals that are needed to operate the processor and provides as output all control signals necessary to execute the instructions. The outputs from the Control Unit are the control signals that we have been using in previous phases to generate control sequences for the instructions of the Mini SRC.

 


Figure 1: Block diagram of the Control Unit

The Control Unit generates the control signals from four principal sources:

- (a) The op-code fields of the IR
- (b) Signals from the Datapath such as CON FF, and the condition code registers (if any)
- (c) Control step information such as signals T0, T1, ...
- (d) External inputs such as Stop, Reset, Done (if memory is slow), and other signals such as interrupts (if any)

The external *Reset* input should get the Mini SRC to an initial state, where all registers including PC in the Datapath are set to 0, the *Run* indicator is set to 1, and the processor starts at Step T0. As the clock continues to run, instructions should be fetched and executed one after the other until a *halt* instruction is encountered, at which point the control stepping process should be halted and the *Run* indicator is set to 0. Note that, the external *Stop* input signal works the same way as the *halt* instruction.

During T0, T1, and T2, the control signals that are asserted to implement the “instruction fetch” sequence are independent of the bits in the Instruction Register. For instance, in Step T0, the control signals PCout, MARin, IncPC and Zin are set to 1. In Step T1, the control signals Zlowout, PCin, Read, and MDRin are set to 1. In Step T2, the control signals MDRout and IRin are set to 1. However, from Step T3 onward, until the current instruction is completed, the control signals that are asserted are a function of both Step Ti and the op-code bits in the IR register.

In the following, you will see two different methods to design your Control Unit. There is a trade-off between the two methods. Method 1 is clearly the easier method, but it may generate more hardware. You are, of course, welcome to come up with your own design.

Method 1: It is possible to write the Verilog/VHDL code without worrying about the combinational logic expressions for each control signal. Therefore, the code will come clean, and the instructions will be executed in the most efficient manner. However, this approach may generate more hardware. The following sample Verilog/VHDL code is provided as a starting point for this method, which you may need to verify and revise for your Control Unit:

// this is the Verilog sample code for Method 1 for the Control Unit

```
`timescale 1ns/10ps
module control_unit (
    output reg    Gra, Grb, Grc, Rin, ..., Rout,      // define the inputs and outputs to your Control Unit here
                  Yin, Zin, PCout, IncPC, ..., MARin,
                  Read, Write, ..., Clear,
                  ADD, AND, ..., SHR,
    input         [31:0] IR,
    input         Clock, Reset, Stop, ..., Con_FF);
    parameter     reset_state = 4'b0000, fetch0 = 4'b0001, fetch1 = 4'b0010, fetch2 = 4'b0011,
                  add3 = 4'b0100, add4 = 4'b0101, add5 = 4'b0110, ...;
    reg           [3:0] present_state = reset_state; // adjust the bit pattern based on the number of states

always @(posedge Clock, posedge Reset) // finite state machine; if clock or reset rising-edge
begin
    if (Reset == 1'b1) present_state = reset_state;
    else case (present_state)
        reset_state:    present_state = fetch0;
        fetch0:         present_state = fetch1;
        fetch1:         present_state = fetch2;
        fetch2:         begin
```

```

                                case (IR[31:27])    // inst. decoding based on the opcode to set the next state
                                    5'b00011: present_state = add3;    // this is the add instruction
                                    ⋮
                                endcase
                            end
                        add3:    present_state = add4;
                        add4:    present_state = add5;
                        ⋮
                    endcase
                end

always @(present_state)    // do the job for each state
begin
    case (present_state)    // assert the required signals in each state
        reset_state: begin
            Gra <= 0; Grb <= 0; Grc <= 0; Yin <= 0;    // initialize the signals
            ⋮
        end
        fetch0: begin
            PCout <= 1;    // see if you need to de-assert these signals
            MARin <= 1;
            IncPC <= 1;
            Zin <= 1;
        end
        add3: begin
            Grb <= 1; Rout <= 1;
            Yin <= 1;
        end
        ⋮
    endcase
end
endmodule

```

-- this is the VHDL sample code for Method 1 for the Control Unit

library ieee;

use ieee.std_logic_1164.all;

```

entity control_unit is    -- define the inputs and outputs to your Control Unit here
    port (Clock, Reset, Stop, ..., CON_FF:    in    std_logic;
          IR:    in    std_logic_vector(31 downto 0);
          Gra, Grb, Grc, Rin, ..., Rout:    out    std_logic;
          Yin, Zin, PCout, IncPC, ..., MARin:    out    std_logic;
          Read, Write, ..., Clear:    out    std_logic;
          ADD, AND, ..., SHR:    out    std_logic);
end control_unit;

```

architecture behavior of control_unit is

type state is (reset_state, fetch0, fetch1, fetch2, add3, add4, add5, ...);

signal present_state: state;

begin

process (Clock, Reset) -- finite state machine

```

        when others =>
            end case;
        end if;
    end process;

    process (IR)
    begin
        ADD_s <= '0'; AND_s <= '0'; ...
        case IR(31 downto 27) is -- inst. decoding based on the opcode
            when "00011" =>
                ADD_s <= '1'; -- this is the add instruction
            when "01010" =>
                AND_s <= '1'; -- this is the and instruction
            :
            when others =>
            end case;
        end process;

    process (Clock, T0, T1, ...)
    begin
        ADD <= ADD_s AND T4; -- control signal assignment
        Zlowout <= T1 OR (T5 AND (AND_s OR OR_s OR ADD_s OR SUB_s OR ...)) OR ...;
        :
    end process;
end behavior;

```

3. Procedure

3.1) Use one of the above methods, or come up with your own design style, and write your Verilog/VHDL code to implement the Control Unit and add to your Datapath.

3.2) Run a functional simulation of the following program on Mini SRC and demonstrate it to one of the TAs. This program is provided to test the control unit and instructions in Mini SRC, except for brnz/brzr Branch and input/output instructions that will be included in the test code for Phase 4.

Encode your program in the memory with the starting address zero. Initialize registers R0 - R15 and the PC to 0 with the *Reset* input signal. Initialize memory locations 0x47 and 0x8E with the 32-bit hexadecimal values 0x94 and 0x34, respectively.

Minimum outputs are IR, PC, MDR, MAR, R0 – R15, HI, and LO. Add any other signals you would like to observe to convince yourself and the TA that your design works fine.

Address	ORG	0	
0	ldi	R2, 0x69	; R2 = 0x69
	ldi	R2, 2(R2)	; R2 = 0x6B
	ld	R1, 0x47	; R1 = (0x47) = 0x94
	ldi	R1, 1(R1)	; R1 = 0x95
	ld	R0, -7(R1)	; R0 = (0x8E) = 0x34
	ldi	R3, 3	; R3 = 3
	ldi	R2, 0x43	; R2 = 0x43

	brmi	R2, 3	; continue with the next instruction (will not branch)
	ldi	R2, 6(R2)	; R2 = 0x49
	ld	R7, -2(R2)	; R7 = (0x49 - 2) = 0x94
	nop		
	brpl	R7, 2	; continue with the instruction at "target" (will branch)
	ldi	R5, 4(R2)	; this instruction will not execute
	ldi	R4, -3(R5)	; this instruction will not execute
target:	add	R2, R2, R3	; R2 = 0x4C
	addi	R7, R7, 3	; R7 = 0x97
	neg	R7, R7	; R7 = 0xFFFFFFFF69
	not	R7, R7	; R7 = 0x96
	andi	R7, R7, 0xF	; R7 = 6
	ror	R1, R0, R3	; R1 = 0x80000006
	ori	R7, R1, 9	; R7 = 0x8000000F
	shra	R1, R7, R3	; R1 = 0xF0000001
	shr	R2, R2, R3	; R2 = 9
	st	0x8E, R2	; (0x8E) = 9 new value in memory with address 0x8E
	rol	R2, R0, R3	; R2 = 0x1A0
	or	R4, R3, R0	; R4 = 0x37
	and	R1, R2, R0	; R1 = 0x20
	st	0x27(R1), R4	; (0x47) = 0x37 new value in memory with address 0x47
	sub	R0, R2, R4	; R0 = 0x169
	shl	R1, R2, R3	; R1 = 0xD00
	ldi	R4, 6	; R4 = 6
	ldi	R5, 0x1B	; R5 = 0x1B
	mul	R5, R4	; HI = 0; LO = 0xA2
	mfhi	R7	; R7 = 0
	mflo	R6	; R6 = 0xA2
	div	R5, R4	; HI = 3, LO = 4
	ldi	R10, 1(R4)	; R10 = 7 setting up argument registers
	ldi	R11, -2(R5)	; R11 = 0x19 R8, R9, R10, and R11
	ldi	R12, 0(R6)	; R12 = 0xA2
	ldi	R13, 3(R7)	; R13 = 3
	jal	R12	; address of subroutine subA in R12 - return address in R15
0x29	halt		; upon return, the program halts
subA:	ORG	0xA2	; procedure subA
0xA2	add	R9, R10, R12	; R8 and R9 are return value registers
	sub	R8, R11, R13	; R9 = 0xA9, R8 = 0x16
	sub	R9, R9, R8	; R9 = 0x93
	jr	R15	; return from procedure

4. Report

Upload your Phase 3 report (one per group) in PDF format to onQ by 11:59pm on the day of your Phase 3 demo. Phase 3 report consists of:

- Your Verilog/VHDL code (and schematic, if any)
- Functional simulation run of the program
- Printouts of the contents of memory before and after the program run